



Using Keypad


Hsi-Pin Ma

<http://lms.nthu.edu.tw/course/21094>

Department of Electrical Engineering

National Tsing Hua University

4x4 Keypad

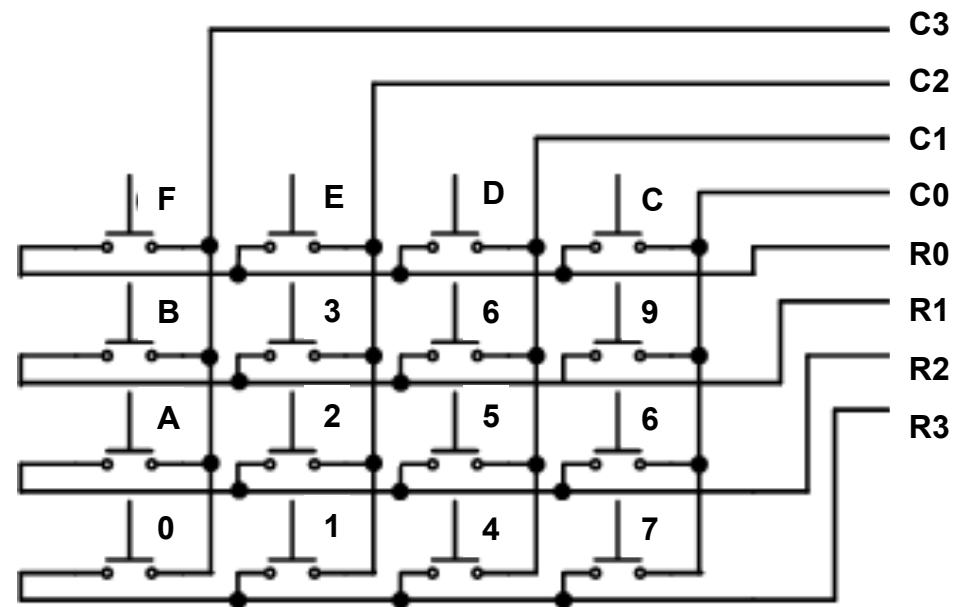


Row[3]	Row[2]	Row[1]	Row[0]
L3	L4	K1	K2
Col[3]	Col[2]	Col[1]	Col[0]
H1	H2	J1	J3

Note

- column, row are all low active
 - 0111 for first row / column
 - 1101 for third row / column
- Use 'row scan' + 'key press (column)' to locate the real key pressed (2D addressing)
- See the demo (keypad_scan) and example for details

Keypad Scan

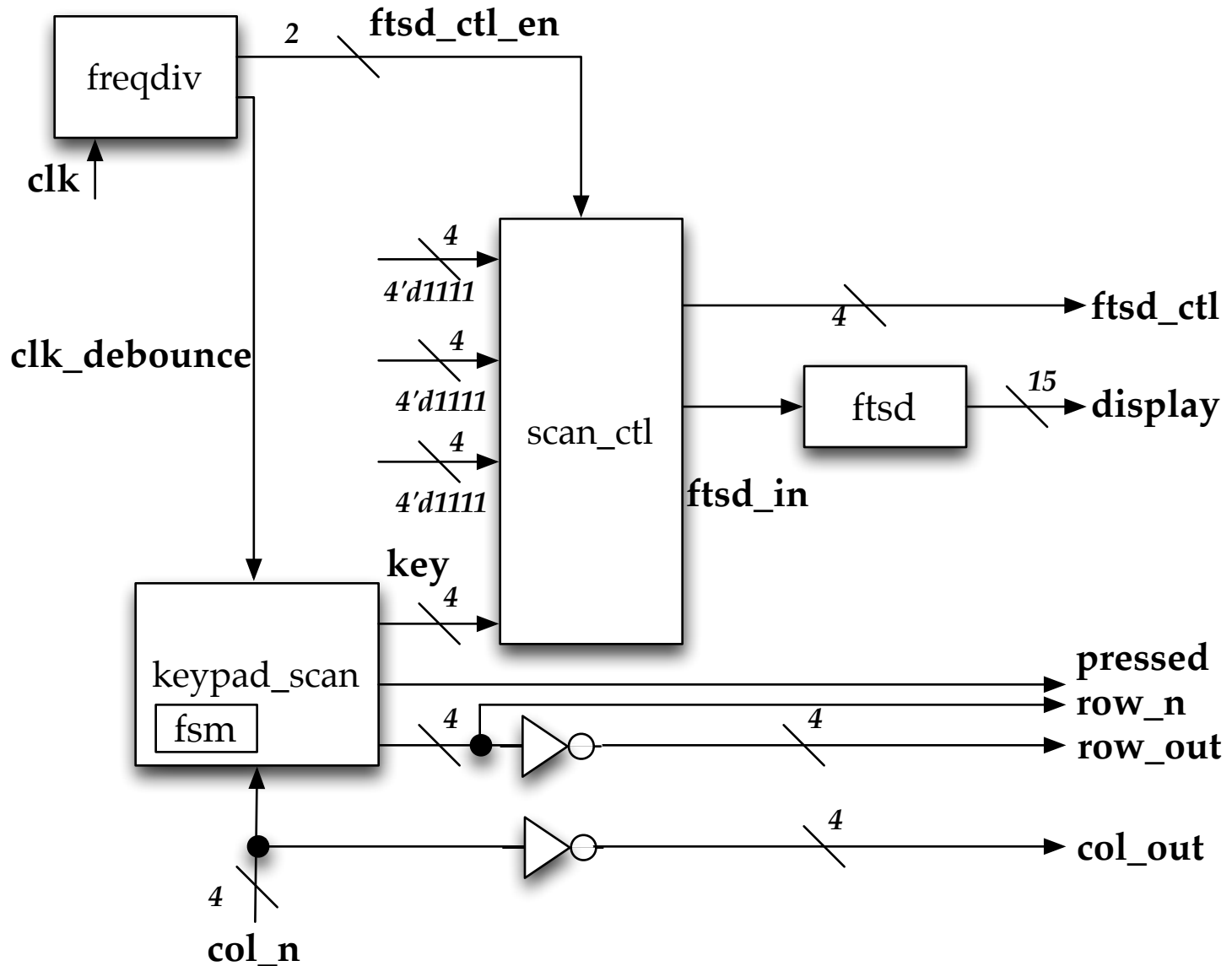

keypad_scan.v

1. Row scan (row_n: 0111->1011->1101->1110, loop every 4 clocks)
2. For {row_n,col_n}, the mapping:

// 1st row

0111_0111 => F

0111_1011 => E

0111_1101 => D

0111_1110 => C

// 3rd row

1101_0111 => A

1101_1011 => 2

1101_1101 => 5

1101_1110 => 8

// 2nd row

1011_0111 => B

1011_1011 => 3

1011_1101 => 6

1011_1110 => 9

// 4th row

1110_0111 => 0

1110_1011 => 1

1110_1101 => 4

1110_1110 => 7

Just one-level case. AVOID using two level (nested) cases.

keypad_scan.v

```

`include "global.v"
module keypad_scan(
    clk, // scan clock
    rst_n, // active low reset
    col_n, // pressed column index
    row_n, // scanned row index
    key, // returned pressed key
    pressed // whether key pressed (1) or not (0)
);

// Declare I/Os
input clk; // scan clock
input rst_n; // active low reset
input [`KEYPAD_COL_WIDTH-1:0] col_n;
output [`KEYPAD_ROW_WIDTH-1:0] row_n;
output [3:0] key; // returned pressed key
output pressed; // whether key pressed (1) or not (0)

// Declare internal nodes
reg [1:0] sel, sel_next;
reg [`KEYPAD_ROW_WIDTH-1:0] row_n;
reg [3:0] key;
reg [3:0] key_detected;
reg [3:0] key_next;
reg keypad_state, keypad_state_next;

```

```

    reg [`KEYPAD_PAUSE_PERIOD_BIT_WIDTH-1:0]
        pause_delay, pause_delay_next;
    reg pressed_detected;
    reg pressed_next;
    reg pressed

// A repetitive counter for row-wise scan
always @(posedge clk or negedge rst_n)
    if (~rst_n)
        sel = 2'b00;
    else
        sel = sel_next;

always @*
    sel_next = sel + 1'b1;

// row-wise scan
always @*
    case (sel)
        2'd0: row_n = 4'b0111;
        2'd1: row_n = 4'b1011;
        2'd2: row_n = 4'b1101;
        2'd3: row_n = 4'b1110;
        default: row_n = 4'b1111;
    endcase

```

keypad_scan.v

```

// column-wise readout
always @*
begin
  case ({row_n,col_n})
    `KEYPAD_DEC_WIDTH'b0111_0111: // press 'F'
    begin
      key_detected = `KEY_F;
      pressed_detected = `KEYPAD_PRESSED;
    end
    `KEYPAD_DEC_WIDTH'b0111_1011: // press 'E'
    begin
      key_detected = `KEY_E;
      pressed_detected = `KEYPAD_PRESSED;
    end
    `KEYPAD_DEC_WIDTH'b0111_1101: // press 'D'
    begin
      key_detected = `KEY_D;
      pressed_detected = `KEYPAD_PRESSED;
    end
    .....
  endcase
end

```

```

`KEYPAD_DEC_WIDTH'b1110_1011: // press '1'
begin
  key_detected = `KEY_1;
  pressed_detected = `KEYPAD_PRESSED;
end
`KEYPAD_DEC_WIDTH'b1110_1101: // press '4'
begin
  key_detected = `KEY_4;
  pressed_detected = `KEYPAD_PRESSED;
end
`KEYPAD_DEC_WIDTH'b1110_1110: // press '7'
begin
  key_detected = `KEY_7;
  pressed_detected = `KEYPAD_PRESSED;
end
default:
begin
  pressed_detected = `KEYPAD_NOT_PRESSED;
  key_detected = `KEY_0;
end
endcase

```

Just one-level case. AVOID using two level (nested) cases.

FSM for Keypad Scan


Red: input

Purple: output

```
keypad_state_next = `SCAN
pressed_next = `KEYPAD_NOT_PRESSED
pause_delay_next = 4'b0
key_next = key
```

pause_delay == 4'b1111
 
```
keypad_state_next = `PAUSE
pressed_next = `KEYPAD_PRESSED
pause_delay_next = pause_delay + 1'b1
key_next = key
```



pressed_detected != 1

pause_delay != 4'b1111

pressed_detected == 1

```
keypad_state_next = `SCAN
pressed_next = `KEYPAD_NOT_PRESSED
pause_delay_next = 4'b0
key_next = key
```

```
keypad_state_next = `PAUSE
pressed_next = `KEYPAD_PRESSED
pause_delay_next = 4'b0
key_next = key_detected
```

default:

```
keypad_state_next = `SCAN
pressed_next = `KEYPAD_NOT_PRESSED
pause_delay_next = 4'b0
key_next = key
```


keypad_scan.v

```
// *****  
// FSM for keypad scan  
// *****  
// FSM state transition  
always @*  
case (keypad_state)  
  `SCAN:  
    begin  
      if (pressed_detected == `KEYPAD_PRESSED)  
        begin  
          keypad_state_next = `PAUSE;  
          pressed_next = `KEYPAD_PRESSED;  
          pause_delay_next = `KEYPAD_PAUSE_PERIOD_BIT_WIDTH'b0;  
          key_next = key_detected;  
        end  
      else  
        begin  
          keypad_state_next = `SCAN;  
          pressed_next = `KEYPAD_NOT_PRESSED;  
          pause_delay_next = `KEYPAD_PAUSE_PERIOD_BIT_WIDTH'b0;  
          key_next = key;  
        end  
      end  
    end  
  end  
end
```

keypad_scan.v

```
`PAUSE:
begin
  if (pause_delay==`KEYPAD_PAUSE_PERIOD_BIT_WIDTH'b1111)
  begin
    keypad_state_next = `SCAN;
    pressed_next = `KEYPAD_NOT_PRESSED;
    pause_delay_next = `KEYPAD_PAUSE_PERIOD_BIT_WIDTH'b0;
    key_next = key;
  end
  else
  begin
    keypad_state_next = `PAUSE;
    pressed_next = `KEYPAD_PRESSED;
    pause_delay_next = pause_delay + 1'b1;
    key_next = key;
  end
end
default:
begin
  keypad_state_next = `SCAN;
  pressed_next = `KEYPAD_NOT_PRESSED;
  pause_delay_next = `KEYPAD_PAUSE_PERIOD_BIT_WIDTH'b0;
  key_next = key;
end
endcase
```

keypad_scan.v

```
// FSM state register
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    keypad_state <= 1'b0;
  else
    keypad_state <= keypad_state_next;

// Keypad Pause state counter
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    pause_delay <= `KEYPAD_PAUSE_PERIOD_BIT_WIDTH'd0;
  else
    pause_delay <= pause_delay_next;

// pressed indicator
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    pressed <= `KEYPAD_NOT_PRESSED;
  else
    pressed <= pressed_next;
```

```
// pressed key indicator
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    key <= `KEY_0;
  else
    key <= key_next;

endmodule
```

Modification for lab6

- You should modify the keypad_scan.v to get the press value correctly.
 - Hint: One pulse pressed?
- Steps for exp.2 demo:
 - After reset
 - Press first number (0-9) and the number will be displayed in ftzd0 (addend)
 - Press A for addition
 - Press second number (0-9) and the number will be displayed in ftzd1(augend)
 - Press E, and the result will be shown on ftzd2, ftzd3