


Lab 1: Introduction to Verilog HDL

103061207 徐安廷


Design Specification

 1. Full Adder

- ✓ Logic Equation: $S = a \oplus b \oplus C_i$, $C_o = a'b + ac_i + bc_i$
- ✓ Logic Diagram:



- ✓ Block Diagram:

 

- ✓ I/O:

Half Adder:

Inputs: a, b.

Outputs: s, co.


Full Adder:

Inputs: a, b, ci.

Outputs: co, s.

2. Single Digit Decimal Adder

- ✓ Block Diagram:

 

- ✓ I/O:


Inputs: a[3:0], b[3:0], ci.

Outputs: result[3:0], s[3:0], co, cout.

3. 2-to-4-Line Decoder

- ✓ Logic Equation: $d[0] = E \cdot in[1]' \cdot in[0]'$, $d[1] = E \cdot in[1]' \cdot in[0]$,
 $d[2] = E \cdot in[1] \cdot in[0]'$, $d[3] = E \cdot in[1] \cdot in[0]$.

- ✓ Block Diagram:

 

- ✓ I/O:
Inputs: E, in[1:0].
Output: d[3:0].

Design Implementation

1. Full Adder

- ✓ a and b is the bit we like to add, and ci is an one bit carry in. s is the result, and co is an one bit carry out.
- ✓ The logic function should be: $s = a \oplus b \oplus C_i$, $co = a'b + ab'$

2. Single Digit Decimal Adder

- ✓ Logic function:
When adding input a and b, if the result is larger than 9, it should add 6 to the result.
So, we will get a one bit carry out and a four-bit binary number result[3:0].
 $C_{out} = K + Z_8Z_4 + Z_8Z_2$

3. 2-to-4-Line Decoder

- ✓ Logic function
E is enable. When E=0, the decoder will output 0000.
 $D[0] = E \& (\sim in[1]) \& (\sim in[0])$
 $D[1] = E \& (\sim in[1]) \& (in[0])$
 $D[2] = E \& (in[1]) \& (\sim in[0])$
 $D[3] = E \& (in[1]) \& (in[0])$

Discussion

- ✓ It was really a happy experiment, only when debugging made me disappointed. The only wrong thing a met is I forgot to link the full adders in the second 4-bit adder. So, it is not weird that the simulation turned out lots of red Xs. The experiment results went all correct, since I follow the references in the hangout, so it ran as I expected.

Conclusion

- ✓ I have got familiar with the use of Verilog, and know how to declare I/Os variables and write a testbench to test my circuit. During the debugging, I tried to understand the error messages. Hope it will help me to finish future projects.

References

- ✓ Teaching handouts <Introduction> p.52:
It helps making a decimal adder without using any if statements, but by only using the simple logic gates to get the goal.