

Lab 1: Introduction to Verilog HDL

Objective

- ✓ Review fundamental logic components.
- ✓ Introduce Verilog HDL modeling and verification.

Prerequisite

- ✓ Fundamentals of logic gates.

Experiments

- 1 Design and implement a full adder. ($s + cout = x + y + cin$)
 - 1.1 Write the logic equation.
 - 1.2 Draw the related logic diagram.
 - 1.3 Verilog RTL representation with verification.
- 2 Design a single digit decimal adder with input $A(a_3a_2a_1a_0)$, $B(b_3b_2b_1b_0)$, $C_{in}(ci)$, and output $S(s_3s_2s_1s_0)$ and $C_{out}(co)$.
- 3 (Bonus) Design a 2-to-4-line decoder with enable (input $in[1:0]$, enable en and output $d[3:0]$).
 - 3.1 Logic equation,
 - 3.2 Logic schematic,
 - 3.3 Verilog RTL representation with verification.

TA: _____