


Lab 2: FPGA Emulation

103061207 徐安廷 An-Ting Hsu

Design Specification

 1. Full Adder


- ✓ Experiment Goal:
Alter the full adder in Lab1-1 to make the calculation result be shown on the LEDs.
- ✓ Block Diagram:



- ✓ I/O:
Inputs: x, y, cin.
Outputs: s, cout.

 2. BCD to 14-Segment Display Decoder

- ✓ Experiment Goal:
Give a BCD code to the FPGA board, and let the 14-segment display show the code in decimal numbers.
- ✓ Block Diagram:



- ✓ I/O:
Inputs: bcd[3:0].
Outputs: led[3:0], display[3:0].

Design Implementation

1. Full Adder

- ✓ Logic Function: $s = x \oplus y \oplus cin$, $cout = x \cdot y \mid x \cdot cin \mid y \cdot cin$
- ✓ I/O Pin Assignment:

x	y	cin	s	cout
T1	P2	P1	H5	H6

2. BCD to 14-Segment Display Decoder

- ✓ I/O Pin Assignment:

bcd[0]~bcd[3]	N2, P1, P2, T1
led[0]~led[3]	F2, F1, H6, H5
display[0]~display[14]	U5, T7, R7, V7, V4, T4, T3, R5, N5, R3, U7, T5, V5, N4, P6

Discussion

- ✓ It has been one of my dream to handle an electrical board. It was excited that I saw the LEDs and 14-segment display showing the result. Since the experiment only need to follow the instruction, I did not meet any bogs or errors.

Conclusion

- ✓ I have got much familiar with the use of Verilog, know how to assign the I/O pins, and how to write my logic program to FPGA. Hope those basic concept and technique may help me in the following labs.

References

1. **Full Adder**
 - ✓ Teaching Handout <FPGA Emulation> p.14~25
→Helps me to learn how to assign the I/O pins.
2. **BCD to 14-Segment Display Decoder**
 - ✓ Teaching Handout <Verilog HDL (2)> p.28
→Telling me how to write the display decoder.